 




Exercise 18: Testing inert_intf on DE0

- We will map your **`inert_intf.sv`** to the DE0-Nano so it can be tested “for real” with an actual inertial sensor. **Work in the same group as Ex17**
- You will create a wrapper **`inert_intf_test`** that contains a few structures to help drive the inert_intf and display the results on LEDs.




Signal	Dir	Description
clk	in	50MHz clock
RST_n	in	Unsynchronized input from push button
LED[7:0]	out	Flopped upper 8-bits of heading
SPI Intf	out/ in	The SS_n, SCLK, MOSI, MISO and INT of SPI interface to 6-axis inertial sensor



 Exercise 18: Testing inert_intf on DE0



- We will map your ***inert_intf.sv*** to the DE0-Nano so it can be tested “for real” with an actual inertial sensor.
- You will create a wrapper ***inert_intf_test*** that contains a few structures to help drive the *inert_intf* and display the results on LEDs.





reset_synch

  - On the FPGA board, we have a couple of push buttons → we will use one as the source for our async reset
- Push button is simply a switch to ground with a pull-up resistor




Imagine what a disaster this implementation of a global reset would be!!



reset_synch

- We want to build a reset synchronizer that takes in the raw push button signal and creates a signal that is deasserted at the negative edge of clock
- It will have the following interface:

Signal	Dir	Description
RST_n	in	Raw input from push button
clk	in	Clock, we use negative edge
rst_n	out	Our synchronized output which will form the global reset to the rest of our chip

 


- Push of button will async reset the 2 FFs
- When button is released, we have a double flop (meta-stability reasons) to produce our global **rst_n**
- Flops are negative edge triggered so our global reset will deassert on the opposite edge of all our other flops

Code this reset synch unit (**reset_synch.sv**)



inert_intf_test State Machine

- After reset, it waits for a 17-bit free running timer to fill, then asserts **strt_cal** and waits for **cal_done**
- While in calibration, it selects 0xA5 to display on LEDs
- Once calibration is done, it displays bits [11:4] of heading on the LEDs
- Only a rest can get it out of DISP state

 



Exercise 18: Testing inert_intf on DE0

- Create **`inert_intf_test.sv`** & test it in ModelSim
- Ensure it compiles in Quartus.
 - There are Quartus project file and settings file available for download (**`inert_intf_test.qpf`**, **`inert_intf_test.qsf`**)
- Each group submits **`inert_intf_test.sv`**, **`inert_intf_test_tb.sv`**
 - Only 1 submission per group of 2 – remember to add 2nd group member in the submission

Demo

- Call anyone on the teaching staff over to demo on a DE0 test platform
 - Bonus credit: +0.5 if your group demos a correct implementation by Friday